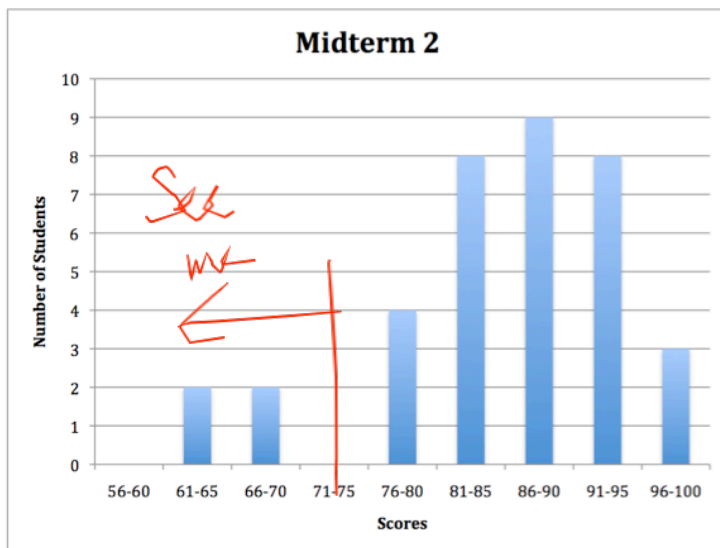


Feb 27

Get Clickers and kits

Web Assign down.

Assignment due Monday



Mean: 85
Std Dev: 9
Median: 86

Tangible: Fill in the Table

Experiment	Effect on Current (be quantitative)	Circle parameter(s) that changed (explain briefly)
Double the length of a Nichrome wire	$i/2$	$n \ A \ u \ \boxed{E}$
Double the cross- sectional area of a Nichrome wire	$2i$	$n \ \boxed{A} \ u \ E$
Two identical bulbs in series compared to a single bulb	$0.7i$	$n \ A \ \boxed{u} \ \boxed{E}$
Two batteries in series compared to a single battery	$2i$	$n \ A \ u \ \boxed{E}$

$$\Delta V = -\int E \cdot d\vec{r}$$

$$= -EL$$

$$E \rightarrow E/2$$

$$i = nA u E$$


$$E \rightarrow E/2$$

u increases

$$\Delta V = -EL$$


$$\oint \Delta V = -2EL$$

Tangible: Mystery circuit

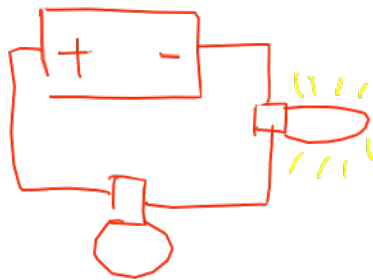

Ponderable: Clicker questions

Q1

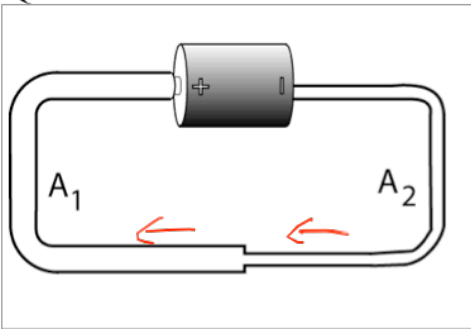
	$A_1 = 4 \cdot A_2$ A) $E_1 = 4 \cdot E_2$ <u>B) $E_1 = (1/4) \cdot E_2$</u> C) $E_1 = (1/16) \cdot E_2$ D) $E_1 = 16 \cdot E_2$ E) Not enough information
--	---

$$I_1 = I_2$$

$$\cancel{A_1} E_1 = \cancel{A_2} E_2$$

$$E_1 = \frac{A_2}{A_1} E_2$$

Q2

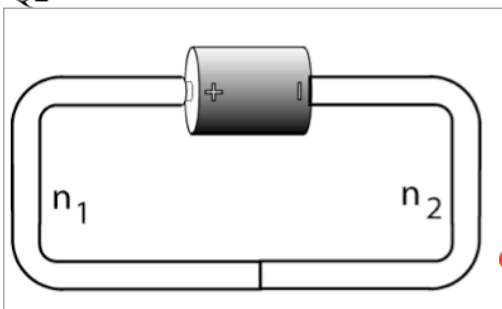	$n_1 = (1/3) \cdot n_2$ A) $E_1 = 3 \cdot E_2$ B) $E_1 = (1/3) \cdot E_2$ C) $E_1 = (1/9) \cdot E_2$ D) $E_1 = 9 \cdot E_2$ <u>E) Not enough information</u>
---	---


$$i_1 = i_2$$

$$n_1 \cancel{A} u_1 E_1 = n_2 \cancel{A} u_2 E_2$$

↓

$$\frac{1}{3} n_2 u_1 E_1 = n_2 u_2 E_2$$


Q3

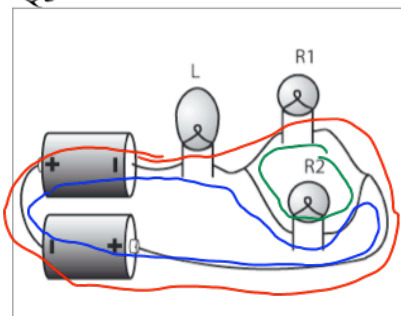	How many different round-trip paths (that go through wires) are there? A) 1 B) 2 C) 3 D) 4 E) more than 4
---	---

Energy Conservation

$$\Delta V = 0 \text{ around closed loop}$$

Q4

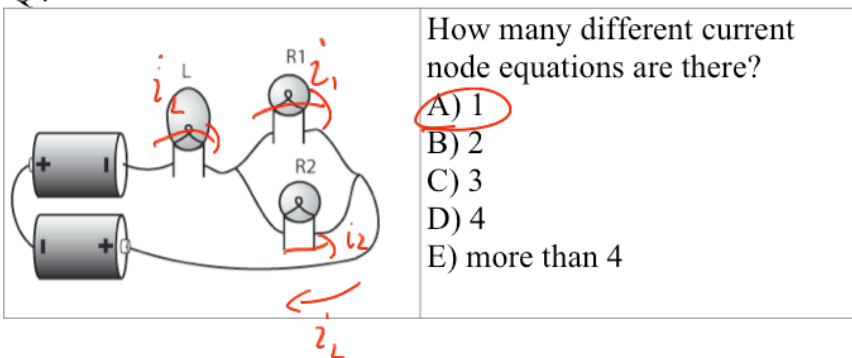


$$i_L = i_1 + i_2$$

Charge Conservation

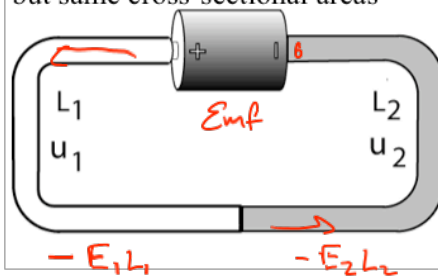Q18.8c

Wires made of different materials,
but same cross-sectional areas




Energy conservation (loop) eqn:

- A) $+\text{emf} - E_1 L_1 - E_2 L_2 = 0$
- B) $+\text{emf} + E_1 L_1 + E_2 L_2 = 0$
- C) $+\text{emf} - E^*(L_1 + L_2) = 0$
- D) $+\text{emf} + E^*(L_1 + L_2) = 0$
- E) None of the above

$$+\mathcal{E}_{mf} - E_1 L_1 - E_2 L_2 = 0$$

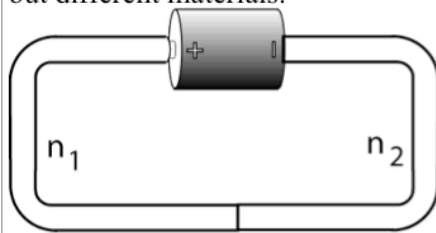Q18.10a

Same length L and cross-sectional area, but different materials.



Same μ 's, but $n_1 = 2 \cdot n_2$

- A) $E_2 = \text{emf}/(1.5 \cdot L)$
- B) $E_2 = \text{emf}/L$
- C) $E_2 = \text{emf}/(2 \cdot L)$
- D) $E_2 = 1.5 \cdot \text{emf}/L$

$$i_1 = i_2$$


$$n_1 \cancel{A_1} \cancel{\mu_1} E_1 = n_2 \cancel{A_2} \cancel{\mu_2} E_2$$

$$2 \cancel{\mu_2} E_1 = \cancel{\mu_2} E_2 \Rightarrow E_1 = \frac{1}{2} E_2$$

$$\text{emf} - E_1 L - E_2 L = 0$$


$$\text{emf} - L \left(\frac{1}{2} E_2 + E_2 \right) = 0 \Rightarrow E_2 = \frac{\text{emf}}{1.5 L}$$

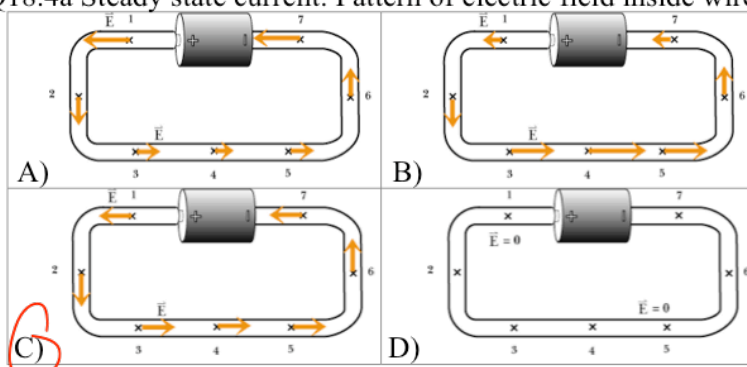Q18.4a Steady state current: Pattern of electric field inside wire?



$$i = n A u E$$

Q4

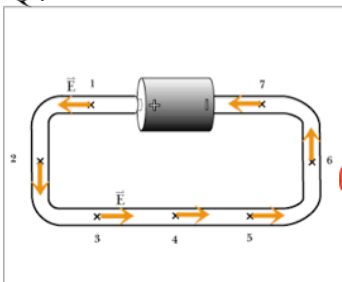	What charges make the electric field inside the wire in this circuit? A) The moving electrons inside the wire B) Charges on the battery and surface of the wire C) Only charges on the battery D) Only charges on the surface of the wire
---	--

Q18.8d

Circuit 1: 1 battery, NiCr wire length L cross-sectional area A electric field E_1 inside wire Circuit 2: 1 battery, NiCr wire length $(3L)$ cross-sectional area A electric field E_2 inside wire.	Which statement is correct? A) $E_1 = E_2$ B) $E_1 = 3 \cdot E_2$ C) $E_1 = E_2/3$
---	---

$$\mathcal{E}_{mf} - E_1 L = 0$$

$$\mathcal{E}_{mf} - E_2 (3L) = 0$$

$$E_1 \cancel{L} = E_2 (3\cancel{L})$$

Q18.8e

Circuit 1: 1 battery, NiCr wire length L cross-sectional area A electric field E_1 inside wire Circuit 2: 1 battery, NiCr wire length L cross-sectional area (4A) electric field E_2 inside wire.	Which statement is correct? A) $E_1 = E_2$ B) $E_1 = 4 \cdot E_2$ C) $E_1 = E_2/4$
---	--

$$\sum \mathcal{E} - E_1 L = 0$$

$$\sum \mathcal{E} - E_2 L = 0$$

$$E_1 L = E_2 L$$

Q18.8f

Circuit 1: 1 battery, NiCr wire length L cross-sectional area A	Which statement is correct? A) $i_1 = i_2$ B) $i_1 = 4 * i_2$ C) $i_1 = i_2 / 4$
Circuit 2: 1 battery, NiCr wire length L cross-sectional area (4A)	

$$i_1 = n A u E_1 \quad E_1 = E_2$$


$$i_2 = n 4A u E_2$$

$$= 4 (n A u E_1)$$

$$= 4 i_1 \Rightarrow i_1 = \frac{i_2}{4}$$

Q18.8b

Wires made of same material

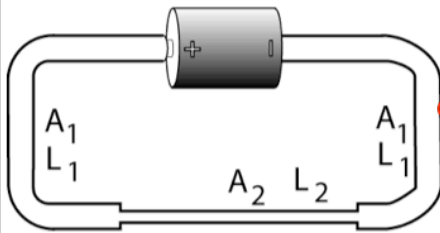


Energy conservation (loop) eqn:

- A) $+emf - E^*(2L_1 + L_2) = 0$
- B) $+emf + E^*(2L_1 + L_2) = 0$
- C) $+emf - 2E_1L_1 - E_2L_2 = 0$
- D) $+emf + 2E_1L_1 - E_2L_2 = 0$
- E) None of the above

Q18.8a

Wires made of same material

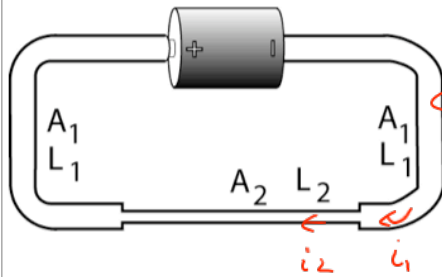


Current conservation (node) eqn:

- A) $i_1 = 2i_2$
- B) $2i_1 = i_2$
- C) $i_1 = i_2$
- D) $i_1 = (A_2/A_1)i_2$
- E) None of the above

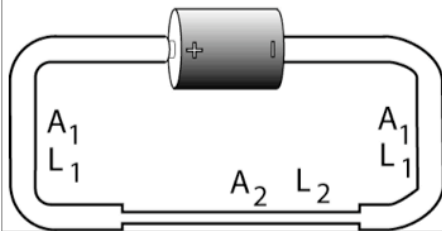Q18.10b

$n = 9 \times 10^{28} \text{ electrons/m}^3$ $u = 7 \times 10^{-5} \text{ (m/s)/(V/m)}$
 $L_1 = 0.2 \text{ m}$ $L_2 = 0.05 \text{ m}$
 $A_1 = 9 \times 10^{-8} \text{ m}^2$ $A_2 = 1.5 \times 10^{-8} \text{ m}^2$



What is E_2 ?

A) 50.4 V/m

B) 12.9 V/m


C) 3.15 V/m

D) 0.788 V/m

E) Not enough information

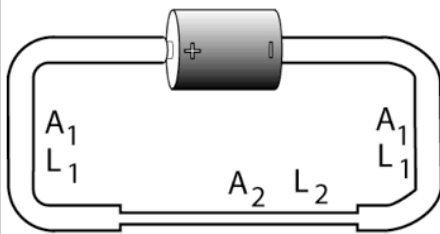Q18.10b Battery emf = 1.5 V

$n = 9e28 \text{ electrons/m}^3$ $u = 7e-5$
(m/s)/(V/m)
 $L_1 = 0.2 \text{ m}$ $L_2 = 0.05 \text{ m}$
 $A_1 = 9e-8 \text{ m}^2$ $A_2 = 1.5e-8 \text{ m}^2$




What must we do to find the current?

- A) Solve for E_1
- B) Solve for E_2
- C) Solve for E_1 and E_2
- D) Not enough information

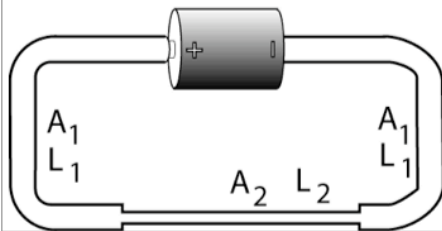Q18.10b Battery emf = 1.5 V

$n = 9 \times 10^{28} \text{ electrons/m}^3$ $u = 7 \times 10^{-5} \text{ (m/s)/(V/m)}$
 $L_1 = 0.2 \text{ m}$ $L_2 = 0.05 \text{ m}$
 $A_1 = 9 \times 10^{-8} \text{ m}^2$ $A_2 = 1.5 \times 10^{-8} \text{ m}^2$




What is E_2 ?

- A) 50.4 V/m
- B) 12.9 V/m
- C) 3.15 V/m
- D) 0.788 V/m
- E) Not enough information

Q18.3b Wires made of same material.

Drift speed of electrons in thick wire vs. drift speed of electrons in thin wire?

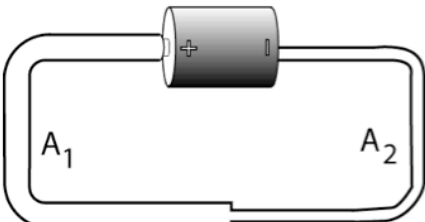	A) $v_1 > v_2$ B) $v_1 = v_2$ C) $v_1 < v_2$ D) Not enough information
---	--

$$i_1 = n A_1 \bar{v}_1$$

$$i_2 = n A_2 \bar{v}_2$$

$$i_1 = i_2$$

$$A_1 \bar{v}_1 = A_2 \bar{v}_2$$