

Mar 2

**Office hours cut short this week: Wed from 10:00-10:30.
If you need to see me, we can set up an appointment for
another time.**

Get Clickers

QUIZ

5. (20 pts) A hydrogen chloride (HCl) molecule consists of a positive ion with charge $+e$ and a negative ion with charge $-e$, separated by a distance of 2×10^{-11} m, as shown in the diagram. Locations 1, 2, 3, and 4 are shown in the diagram. **Note that the diagram is not to scale.**

- (a) (12 pts) Location 1 is 2×10^{-8} m from the center of the molecule, and location 2 is 3×10^{-8} m from the center of the molecule. Calculate the potential difference $V_2 - V_1$, both magnitude and sign. *Show all steps in your work.*


$$\begin{aligned}
 V_2 - V_1 &= - \int_1^2 \vec{E} \cdot d\vec{l} \\
 &= - \int_1^2 (-E_x) dx \\
 &= \frac{1}{4\pi\epsilon_0} 2qs \int_1^2 \frac{dx}{x^3} \\
 &= \frac{1}{4\pi\epsilon_0} 2qs \left(\frac{-1}{2x^2} \right)_1^2 \\
 &= 9 \times 10^9 \times 1.6 \times 10^{-19} \times 2 \times 10^{-11} \left[-\frac{1}{(3 \times 10^{-8})^2} + \frac{1}{(2 \times 10^{-8})^2} \right] = 4.0 \times 10^3 \text{ V}
 \end{aligned}$$

- (b) (8 pts) Location 3 is 2×10^{-8} m from the center of the molecule, and location 4 is 3×10^{-8} m from the center of the molecule. Calculate the potential difference $V_4 - V_3$, both magnitude and sign. *Show all steps in your work.*

$$\vec{E} \cdot d\vec{\ell} = 0$$

$$\int \vec{E} \cdot d\vec{\ell} = 0$$

$$V_4 - V_3 = 0$$

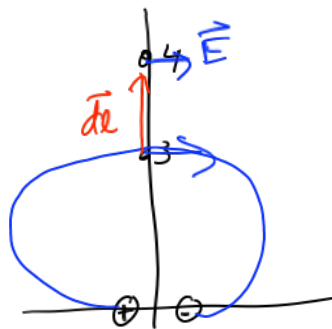

Q18.10b Battery emf = 1.5 V

$n = 9 \times 10^{28}$ electrons/ m^3 $u = 7 \times 10^{-5}$
(m/s)/(V/m)

$L_1 = 0.2$ m

$L_2 = 0.05$ m

$A_1 = 9 \times 10^{-8}$ m^2

$A_2 = 1.5 \times 10^{-8}$ m^2


What must we do to find the current?

A) Solve for E_1

B) Solve for E_2


C) Solve for E_1 and E_2

D) Not enough information

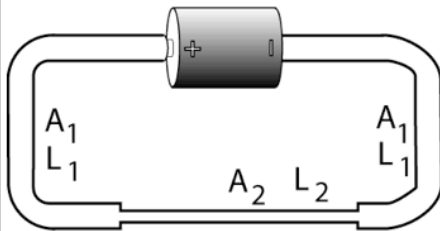

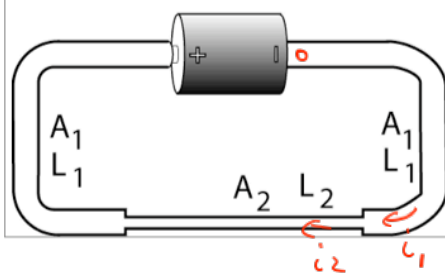Q18.10b Battery emf = 1.5 V

$n = 9e28$ electrons/ m^3 $u = 7e-5$
 (m/s)/(V/m)
 $L_1 = 0.2$ m $L_2 = 0.05$ m
 $A_1 = 9e-8$ m^2 $A_2 = 1.5e-8$ m^2



What is E_2 ?

- A) 50.4 V/m
- B) 12.9 V/m
- C) 3.15 V/m
- D) 0.788 V/m
- E) Not enough information

$$i_1 = i_2$$

$$n A_1 u E_1 = n A_2 u E_2$$

$$E_1 = \frac{A_2}{A_1} E_2$$

$$\Delta V = 0 = +\mathcal{E}_{\text{emf}} - E_1 L_1 - E_2 L_2 - E_1 L_1 = (+\mathcal{E}_{\text{emf}} - 2E_1 L_1 - E_2 L_2 = 0)$$

$$\left(2 \frac{A_2}{A_1} E_2 L_1 + E_2 L_2 \right) = \mathcal{E}_{\text{emf}}$$

$$E_2 = \frac{\mathcal{E}_{\text{emf}}}{2 \frac{A_2}{A_1} L_1 + L_2} = 12.9 \text{ V/m}$$

Discussion: Summary



for steady state

\vec{E} is parallel to wire

\vec{E} is constant along wire (for same geometry + material)

\vec{E} is const across wire's diameter

Tangible: Do charges from the battery drive i ?

Charges on surface of wire + battery


Q2: What makes current flow in a circuit?

A) Electrons push each other through the wire

B) Since there is no friction, no force is needed to keep electrons moving


C) A nonzero electric field inside the wire keeps the electrons moving

Ponderable: Squiggly Circuit

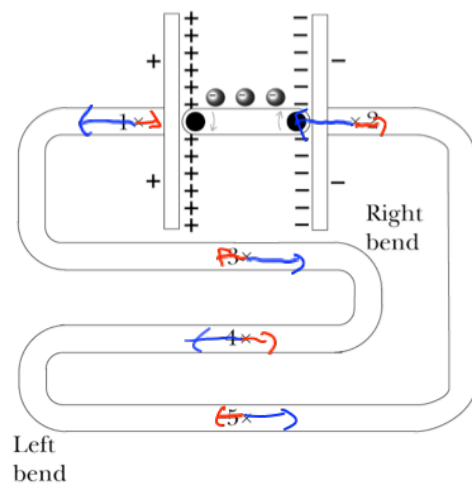

\vec{v} = drift velocity
 \vec{E}

Ponderable: Squiggly Circuit

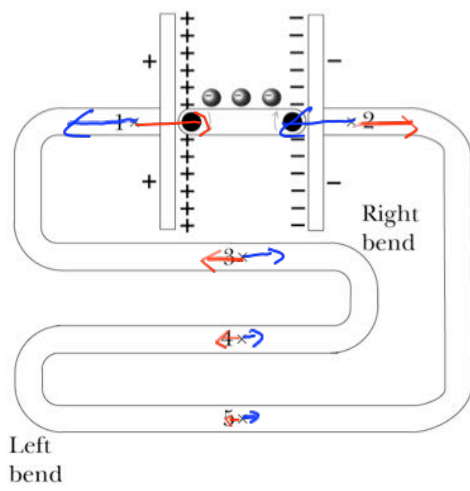

$$\vec{E}$$

$$\vec{V} = u\vec{E}$$

Wiggly