

Mar 6

Get Clickers, kits, and stopwatch

Minilab: Charging and Discharging a Capacitor

Fade Away

Clicker Questions:

Effect of size combinations:

What happens to the capacitance if the area of a capacitor doubles?

- A. doubles
- B. halves
- ~~C. stays the same~~



$$Q = C \Delta V$$

$$\Delta V = E d$$
$$= \frac{Q/A}{\epsilon_0} d$$



$$Q = C \frac{A}{d} \epsilon_0$$

$$C = \frac{A \epsilon_0}{d}$$

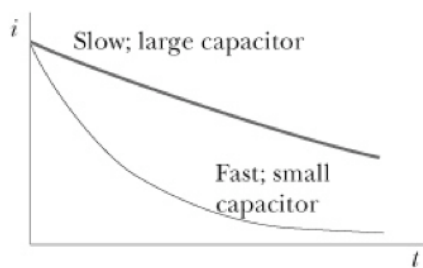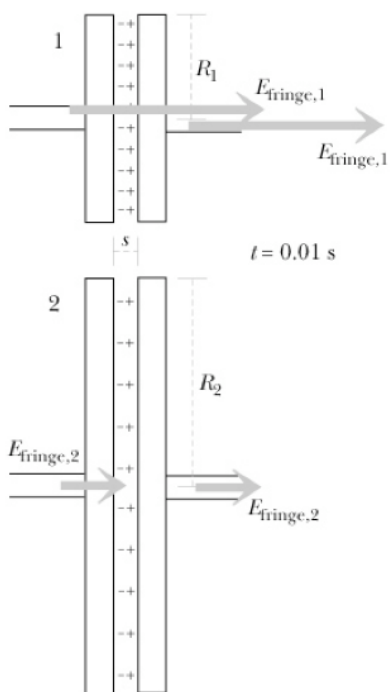


What happens to the capacitance if the separation of a capacitor is cut in half?

A. doubles


B. halves

C. stays the same

$$C = \frac{A\epsilon_0}{d}$$

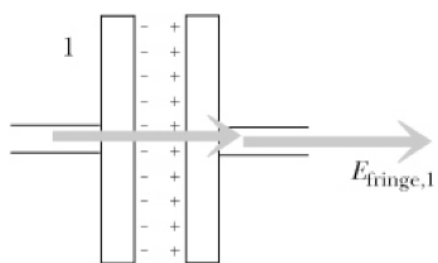


$t = 0.01 \text{ s}$

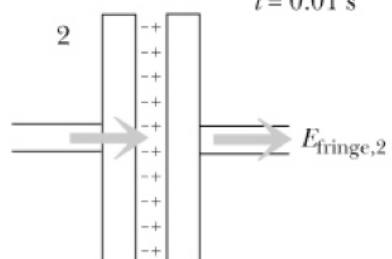

What happens to the capacitance if a dielectric is inserted into a capacitor?

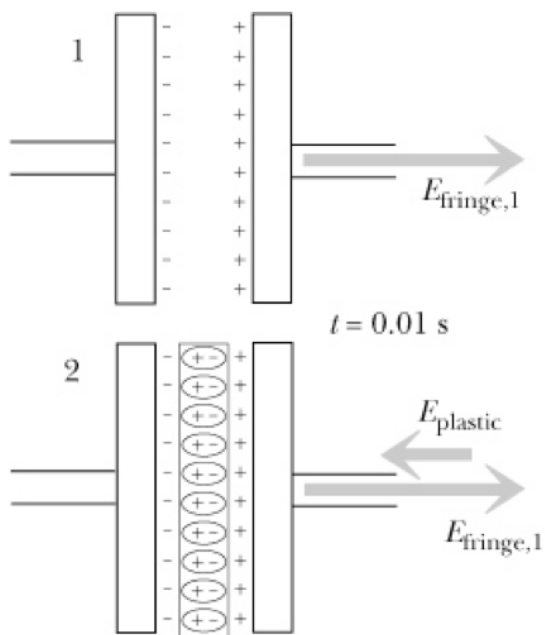- A. Goes up
- B. Goes down
- C. stays the same





Net E_{field}
is smaller

$$E \sim \Delta V$$

$$Q = C \Delta V$$

$$\Rightarrow C = \frac{Q}{\Delta V}$$

bigger $\nearrow$ smaller $\nearrow$

Discussion: Definition of Resistance

Micro Analysis

looking at fundamental
behavior

Hard to measure directly
no electron mobility meter

Micro

$$I = |q| n A u E = (|q| n u) (A E)$$

↑ prop of material ↑ external parameters

$$J = \text{Current density} = \frac{I}{A} = \frac{(|q| n u) \cancel{A} E}{\cancel{A}} = \underbrace{(|q| n u)}_{\sigma} E$$

$$\vec{J} = \sigma \vec{E}$$

↳ Ohm's law

Macro Analysis

Measure contributions
of fundamental quantities


Easy to measure
(Current, volt, ...)

Microscopic view Resistor in uniform field

$$\Delta V = - \int \vec{E} \cdot d\vec{\ell}$$

$$= -EL = -\frac{J}{\sigma} L = -\frac{I/A}{\sigma} L$$

$$|\vec{E}| = \frac{|\vec{J}|}{\sigma}$$

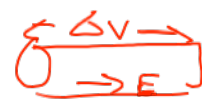

$$|\Delta V| = \left(\frac{L}{\sigma A} \right) I$$


→ define to be resistance $R = \frac{L}{\sigma A}$

$\Delta V = IR \rightarrow$ only true for Ohmic resistors

Non-ohmic:

Capacitor
bulbs
batteries

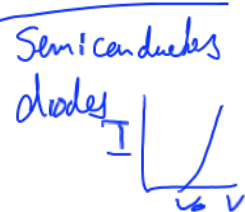$\Delta V \propto I \Rightarrow Q \propto \Delta V$
temp changes conductivity
 $\Delta V \sim \text{const}$ I is not



Micro

$$\vec{v} = u \vec{E}$$


$$i = n A u E$$

macro

$$\vec{J} = \sigma \vec{E}$$

$$I = \frac{\Delta V}{R} \quad \text{ohm's law}$$

Discussion: RC circuit

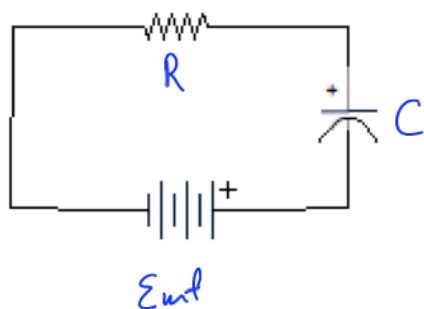

$$\Delta V = 0$$

$$+E_{mf} - \frac{Q}{C} - IR = 0$$

$$I = \frac{E_{mf} - Q/C}{R} = \frac{dQ}{dt}$$

$$\frac{dQ}{dt} = \frac{CE_{mf} - Q}{RC}$$

$$\frac{dt}{RC} = \frac{dQ}{CE_{mf} - Q}$$

$$-\frac{t}{RC} + \text{const} = \ln(CE_{mf} - Q)$$


$$\rightarrow CE_{mf} - Q = Ae^{-t/RC}$$

$$Q = CE_{mf} - Ae^{-t/RC}$$

$$t=0 \quad Q=0 \Rightarrow A = CE_{mf}$$

$$Q = CE_{mf}(1 - e^{-t/RC})$$
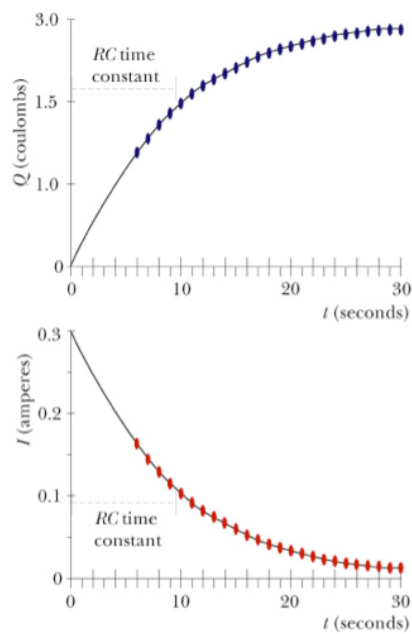
$$I = \frac{dQ}{dt} = \frac{E_{mf}}{R} e^{-t/RC}$$



RC is time
const

$$I = \frac{\mathcal{E}_{\text{mf}}}{R} e^{-t/RC}$$


when $t = RC$

$$I = \frac{\mathcal{E}_{\text{mf}}}{R} e^{-1} = I_0 e^{-1}$$

$$e^{-1} \approx 0.37$$

Tangible: 2 Capacitors and Isolated Bulb


Hold It

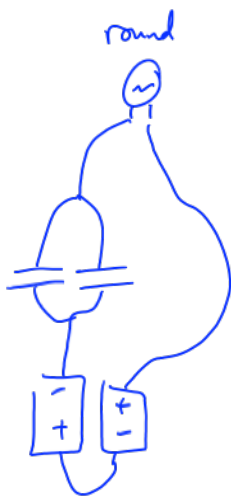

Clicker questions:

Battery in series with bulb. When you disconnect the battery, what happens to the bulb?

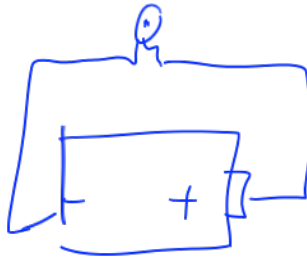- A. stays lit
- ☒ B. turns off
- C. goes dim
- D. brightens



Battery, bulb and capacitor in parallel. When you disconnect the battery, what happens to the bulb?

- A. stays lit**
- B. turns off**
- C. goes dim**
- D. brightens**



Tangible: Usefulness of a Capacitor



Safety Net

Figure 19.12