A REAL, NON-IDEAL BATTERY

Recorder	Manager
Skeptic	Energizer

Real vs. ideal circuit elements

- For an "ideal", ohmic resistor, $\Delta V_{res} = RI$ with *R* constant, no matter how big the current through the resistor is. In an earlier circuit experiment, you found that the resistance of a light bulb was different when it was dim and when it was bright, so the light bulb was not an ideal ohmic resistor.
- Similarly, for an "ideal" battery, ΔV_{batt} is always equal to the emf (determined by chemical reactions).
- However, due to resistance inside the battery, ΔV_{batt} of a real battery is not always equal to emf.
- A real battery can be modeled approximately by treating it as an ideal battery in series with "internal resistance" r_{int} as shown in the diagram below, so $\Delta V_{batt} = \text{emf} r_{int}I$.

Battery properties you will determine in this experiment:

- You will determine the internal resistance r_{int} of your battery.
- You will determine the maximum current your battery can deliver. (An ideal battery could theoretically deliver infinite current, which is impossible.)
- Assemble a series circuit as shown in the diagram with one battery, a high-current ammeter capable of handling 10 amperes, and a long thin Nichrome wire. Place a voltmeter to read the potential difference across the battery.





- Vary the length of the thin Nichrome wire by sliding the contacts, thereby changing its resistance.
- Don't burn yourself on the hot wire!
- Observe the behavior of the potential difference ΔV_{batt} across the battery as the current *I* increases.
- Explain this briefly and qualitatively in terms of the model for a real battery that $\Delta V_{\text{batt}} = \text{emf} r_{\text{int}}I$:

As *I* increases, what happens to ΔV_{batt} ? Why? Explain briefly.

Is ΔV_{batt} greater than, equal to, or less than emf?

Determine the emf

• If I = 0, $\Delta V_{\text{batt}} = \text{emf}-0 = \text{emf}$. Measure the emf of the battery by making *I* be equal to 0. emf = How did you make *I* be zero?

Is your value for the emf consistent with the approximate value printed on the battery?

Measure ΔV_{batt} when there is a large current

- Remove the resistive Nichrome wire and get ready to connect the ammeter directly to the battery.
- VERY BRIEFLY, so as not to deplete the battery too much, measure ΔV_{batt} and the large current *I*.

I =

 $\Delta V_{\text{batt}} =$

Is ΔV_{batt} equal to the emf of this real, non-ideal battery?

Determine the internal resistance of the battery

- Use your data to calculate the internal resistance of the battery. Show your calculations.
- Remember, the potential difference across a real battery is $\Delta V_{\text{batt}} = \text{emf}-r_{\text{int}}I$, not $\Delta V = RI$.

 $r_{\rm int} =$

(Show calculations)

Calculate the maximum current the battery can deliver

• Now that you know the internal resistance of the battery, calculate the maximum possible current this battery can deliver. (Hint: What is the minimum possible ΔV_{batt} ?)

 $I_{\rm max} =$

(Show calculations)

A footnote: What is the resistance of the ammeter?

• The ammeter has some resistance, which is why the current you observed was less than I_{max} .

• You have enough data to determine the resistance of the ammeter. What is R_{ammeter} ?

 $R_{\text{ammeter}} =$

(Show calculations)

Check your work with a neighboring group, then both groups check with instructor. The instructor will look for all questions having been addressed. Turn in report.